

## Measuring Voltage

1. A voltmeter tells us the **strength of the force** pushing electrons from one point in a circuit to another.
2. A voltmeter has a **very high resistance**. Electric current can **not flow through a voltmeter**.
3. A voltmeter is always connected in **parallel** with other components.
4. Voltage is also called **potential difference**.